



Province of the
EASTERN CAPE
EDUCATION

**NATIONAL
SENIOR CERTIFICATE**

GRADE 11

NOVEMBER 2016

**ELECTRICAL TECHNOLOGY
MEMORANDUM**

MARKS: 200

This memorandum consists of 10 pages.

QUESTION 1: OCCUPATIONAL HEALTH AND SAFETY, TOOLS AND MEASURING INSTRUMENTS

- 1.1 Good housekeeping will ensure a safer and better organised workshop. A safer working environment allows for better profits, higher productivity, a happier workforce and saves time. ✓✓ (2)
- 1.2
- Failure to wear protective clothing. ✓
 - Horseplay in the workshop. ✓ (Any two relevant answers.) (2)
- 1.3 A badly planned/unorganised workshop. ✓ (Any relevant answer.) (1)
- 1.4
- To measure AC and DC voltage. ✓
 - Analyse relationship between waveforms. ✓
 - Measure the frequency of the waveforms. ✓ (3)
- 1.5
- An insulation resistance tester can measure very high resistance as required by the Code of Practice. ✓
 - The voltage to be used to test insulation levels should be double the supply voltage. ✓ (2)

[10]

QUESTION 2: SINGLE-PHASE AC GENERATION AND SINGLE-PHASE TRANSFORMERS

- 2.1
- Alternating current is when the current reverses its direction at constant intervals of time. ✓
 - Direct current is when the current flows in one direction only. ✓ (2)
- 2.2 Root-Mean-Square is the amount of DC that is required for producing the same heat as a AC waveform. ✓✓ (2)
- 2.3
- $$\begin{aligned}\Phi &= BA \quad \checkmark \\ &= 3 \times (900 \times 10^{-6}) \quad \checkmark \\ &= 2,7 \text{ mWb} \quad \checkmark\end{aligned}$$
- (3)
- 2.4
- $$\begin{aligned}V_{AVE} &= 0,637 \times V_{Max} \quad \checkmark \\ &= 0,637 \times 16 \quad \checkmark \\ &= 10,19 \text{ V} \quad \checkmark\end{aligned}$$
- (3)
- 2.5
- $$\begin{aligned}EMF &= Blv \sin \theta \quad \checkmark \\ &= 0,08 \times 0,3 \times 50 \sin 90^\circ \quad \checkmark \\ &= 1,2 \text{ V} \quad \checkmark\end{aligned}$$
- (3)
- 2.6
- $$\begin{aligned}V_{RMS} &= V_{MAX} \times 0,707 \\ V_{MAX} &= \frac{V_{RMS}}{0,707} \quad \checkmark \\ &= \frac{240}{0,707} \quad \checkmark \\ &= 339,46 \text{ V} \quad \checkmark\end{aligned}$$
- (3)

- 2.7
- RMS voltage is the DC voltage that will produce the same heat as equivalent AC voltage. ✓
 - Average voltage is just an average value of voltage across a certain time of fluctuations of positive half cycle. ✓ Full wave average value is 0 volt. ✓
- (3)

2.8

$$\begin{aligned} V_{RMS} &= V_{MAX} \times 0,707 \checkmark \\ &= 75 \times 0,707 \checkmark \\ &= 53,03 V \checkmark \end{aligned}$$

$$\begin{aligned} V_{AVE} &= V_{MAX} \times 0,637 \checkmark \\ &= 75 \times 0,637 \checkmark \\ &= 47,78 V \checkmark \end{aligned}$$

(6)


2.9 Lamination is done to reduce eddy current. ✓✓ (2)

2.10 $F = \frac{p \times n}{60} \checkmark$

$$= \frac{2 \times 3\,600}{60} \checkmark$$
$$= 120 \text{ Hz} \checkmark$$

(3)

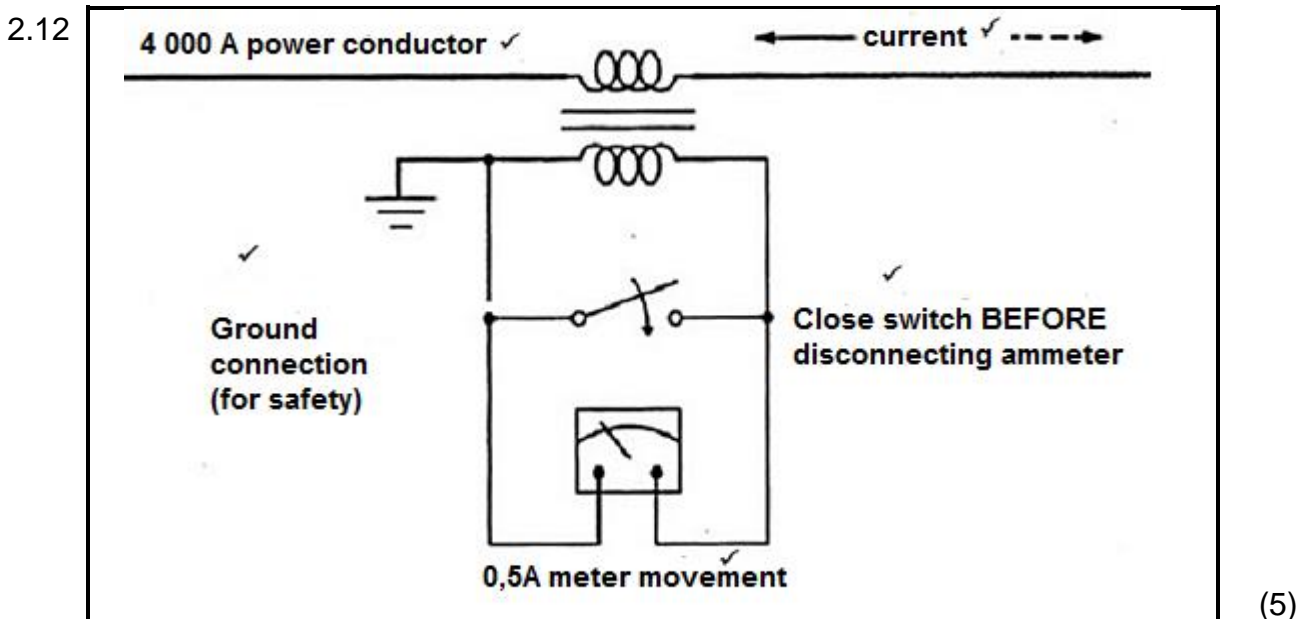- 2.11
- A transformer consists of two coils, a primary and a secondary which are supported by a core. ✓
 - These coils are electrically separated. ✓
 - The basic operation of transformer is based on mutual induction. ✓
 - An AC voltage is applied across the primary windings. ✓
 - A magnetic field build up and collapses in the primary coil. ✓
 - This building up and collapses of the magnetic field in the primary coil cuts the secondary windings, induces an alternating voltage. ✓
 - This induced secondary voltage can be more or less than the supply voltage. ✓
- (Any 6 x 1) (6)




- 2.13 2.13.1 1. Fuse ✓
2. Potential Transformer (PT) ✓
3. Ground connection for safety ✓ (3)
- 2.14 Iron losses ✓
Copper losses ✓
Stray losses ✓ (Any three relevant answers) (3)
- 2.15 • Transmission and distribution over long distances. ✓
• High voltage direct current power transmission. ✓
• Low voltage direct current power sources. ✓
• Electrical furnaces in steel factories. ✓ (Any relevant answers) (3)

[50]**QUESTION 3: SINGLE-PHASE MOTORS AND PROTECTIVE DEVICES**

- 3.1 To automatically disconnect the supply in the event of an overload. ✓✓ (2)
- 3.2 • Bimetal strip ✓
• Electronic digital overload ✓
• Eutectic alloy ✓ (3)
- 3.3 To prevent the restarting of the motor after a power failure. ✓✓ (2)
- 3.4 • The bimetal strip is made up of two different metals bonded together. ✓
• The two metals have different thermal expansion characteristics. ✓
• The bimetal strip bends at a given rate when heated.
• In an overload condition, the heat generated by the heater will cause the bimetal strip to bend until the mechanism is tripped, stopping the motor. ✓ (4)


3.5

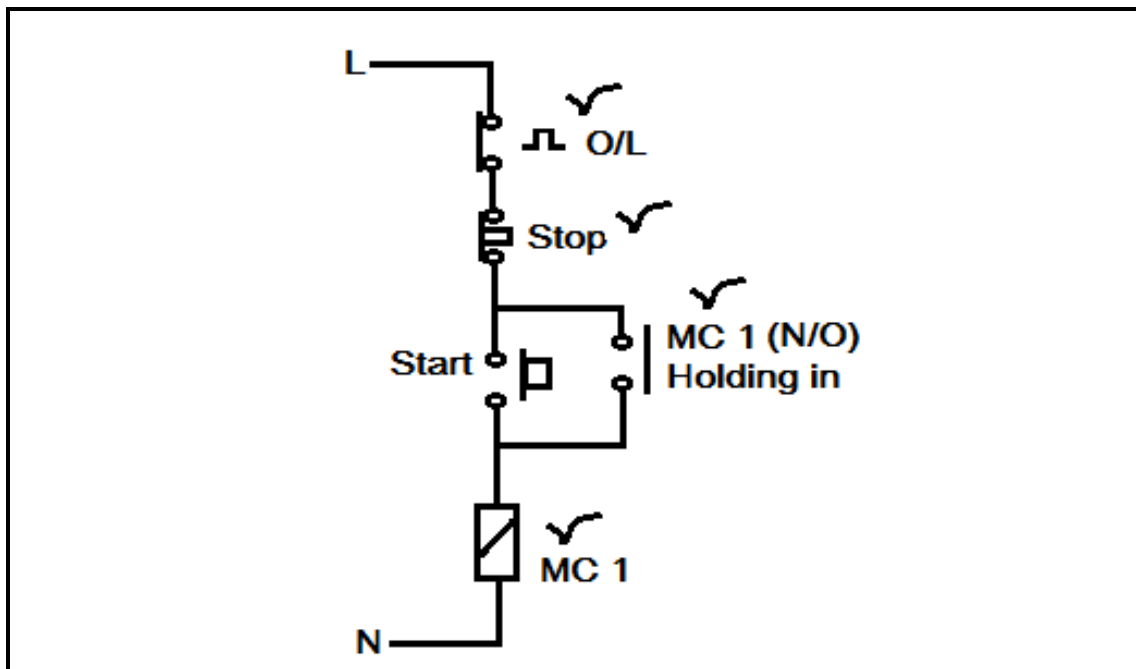

(4)

- 3.6 • Capacitor start motor ✓
• Universal motor ✓ (Any two relevant answers) (2)

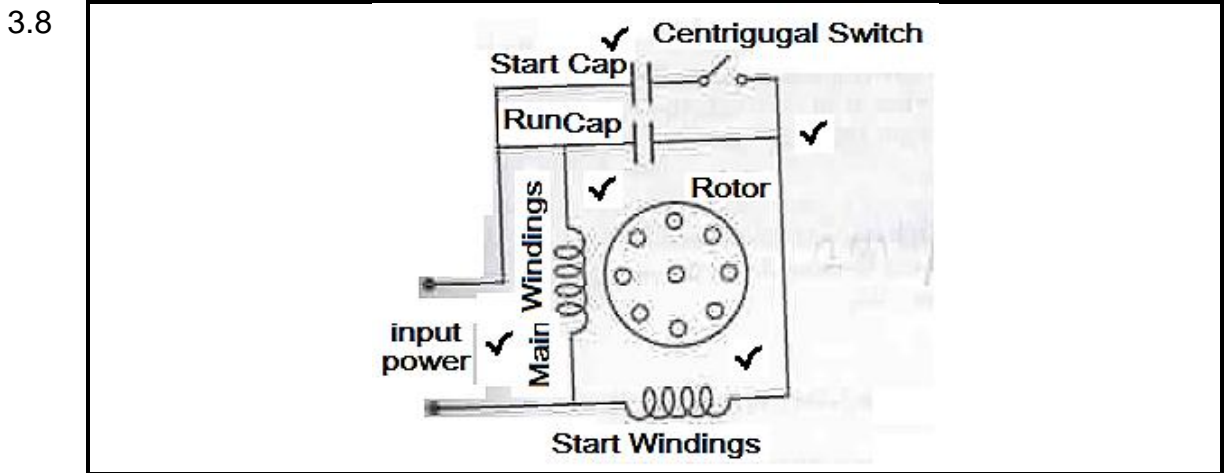3.7 To ensure that there are no leakage/ ✓ short between the windings and earth. ✓ (6)



3.9 By swapping the start windings ✓ with respect to the main windings, but NOT both. ✓ (2)

- 3.10
- Mechanical test ✓
 - Electrical test ✓
- (2)


- 3.11
- Small grinders ✓
 - Small fans ✓
- (2)

[30]


QUESTION 4: SEMI-CONDUCTOR DEVICES, POWER SUPPLIES, AND AMPLIFIERS

- 4.1
- Diode must be removed from the circuit before testing. ✓
 - Diode should be tested in both directions and it should only give a reading in one direction and it is acceptable. ✓
- (2)

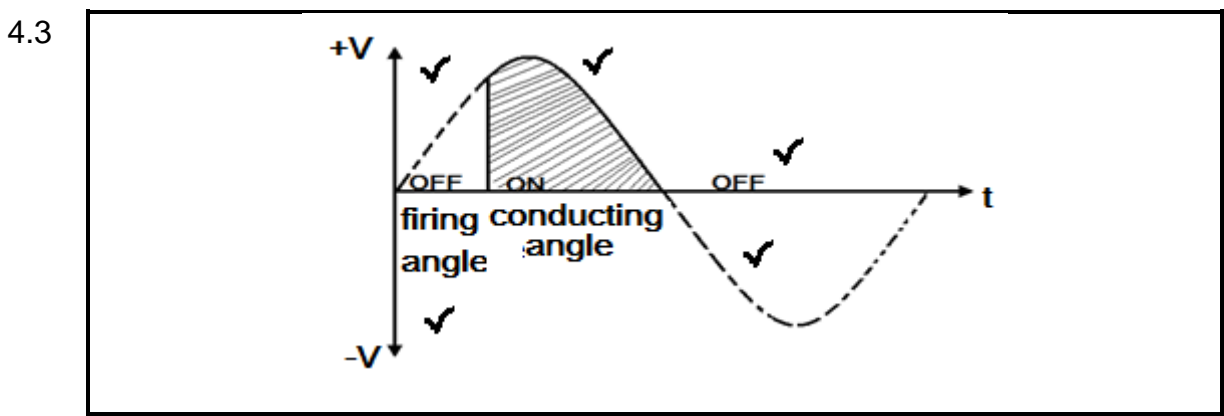- 4.2
- Cut-off ✓
 - Active ✓
 - Saturation ✓
- (3)



4.4

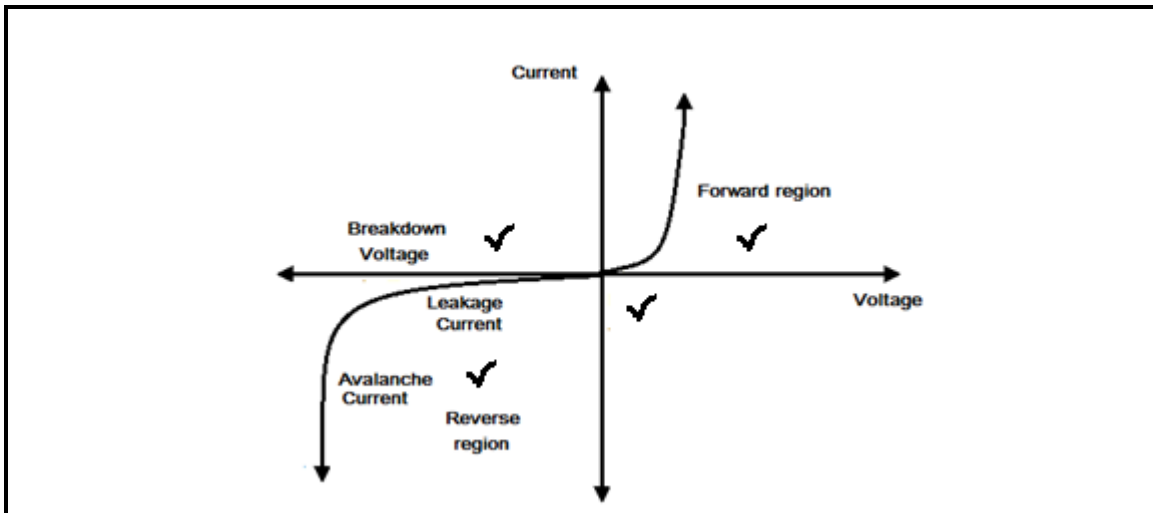

(4)

4.5 During the night:


1. The resistance of the LDR is high. ✓
2. Therefore V_{LDR} is high. ✓
3. But $V_{BE} = V_{LDR}$ so the $V_{BE} \geq 0,6$ V. ✓
4. Transistor will be switched on maximum. ✓
5. Maximum current flows through the LED and the transistor. ✓
6. The LED will be on. ✓

(6)

4.6 It needs a continually changing magnetic field to cut the windings and induce a current. ✓✓

(2)

4.7

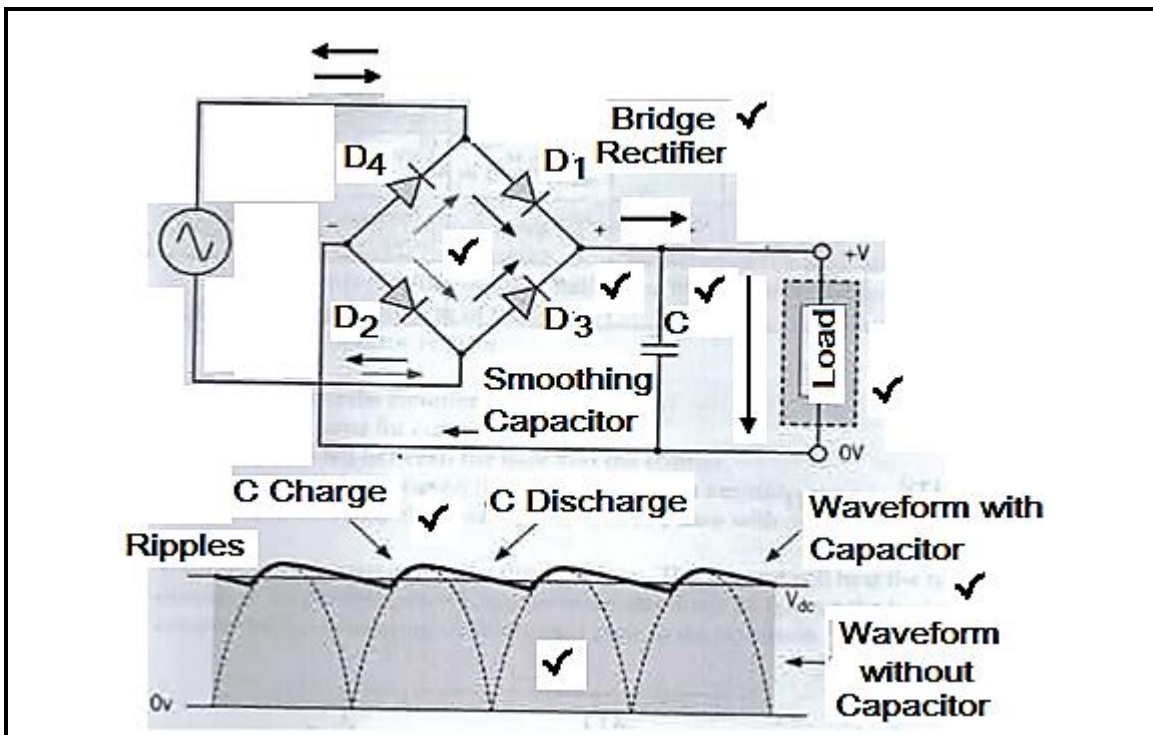

(8)

- 4.8 4.8.1 12 V ✓ (1)
- 4.8.2 7,7 mA ✓ (1)
- 4.8.3 $I_{gain} = \frac{\Delta I_c}{\Delta I_b}$ ✓
- $$= \frac{7,7 \text{ mA} - 2 \text{ mA}}{80 \mu\text{A} - 20 \mu\text{A}} \checkmark$$
- $$= 95 \checkmark \quad (3)$$
- 4.8.4 80 μ A ✓ (1)
- 4.9
- Common base ✓
 - Common emitter ✓
 - Common collector ✓
- (3)
- 4.10 Negative feedback is when a portion of the output is fed back to the input, ✓ and the point at which the input and feedback signals meet there is a phase shift of 180°. ✓ (2)
- 4.11
- Reduce noise and distortion at the output. ✓
 - Enables us to design for a specific gain. ✓
 - Stabilises voltage gain. ✓
- (7)
- 4.12
- Class A ✓ – one transistor amplifies the entire input signal. ✓
 - Class B ✓ – one transistor only amplifies half of the input signal i.e. only the positive half cycle. ✓
 - Class AB ✓ – This fits in between the class A and class B. More than 50% but less than 100% of the input signal is amplified. ✓
 - Class C ✓ – less than 50% of the input signal is amplified. ✓ (Any 3 x 1) (3)

[50]

QUESTION 5: RLC

- 5.1 • Current is maximum. ✓
 • Impedance is minimum. ✓ (Any 2 x 1) (2)

5.2 Impedance is the total opposition a circuit consists of resistor, inductor and capacitor offers to the flow current. ✓✓ (2)

5.3 5.3.1 At resonant $X_L = X_C$
 $X_L = 2\pi fL$ ✓
 $= 2\pi \times 50 \times 0,0637$ ✓
 $= 20,01 \Omega$ ✓ (3)

5.2 5.3.2 $Z = R$
 $Z = 15 \Omega$ ✓ (1)

5.4 5.4.1 $X_C = \frac{1}{2\pi fC}$
 $= \frac{1}{2\pi \times 50 \times 220 \times 10^{-6}}$ ✓
 $= 14,47 \Omega$ ✓


$$X_L = 2\pi fL$$

$$= 2\pi \times 50 \times 75 \times 10^{-3}$$

$$= 23,56 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{22^2 + (23,56 - 14,47)^2} = 23,8 \Omega$$
 (4)

5.4.2 $\cos \theta = \frac{R}{Z}$
 $\theta = \cos^{-1} R/Z$ ✓
 $= \cos^{-1} (22 / 23,8)$ ✓
 $= 22,43^\circ$ lagging ✓ (3)

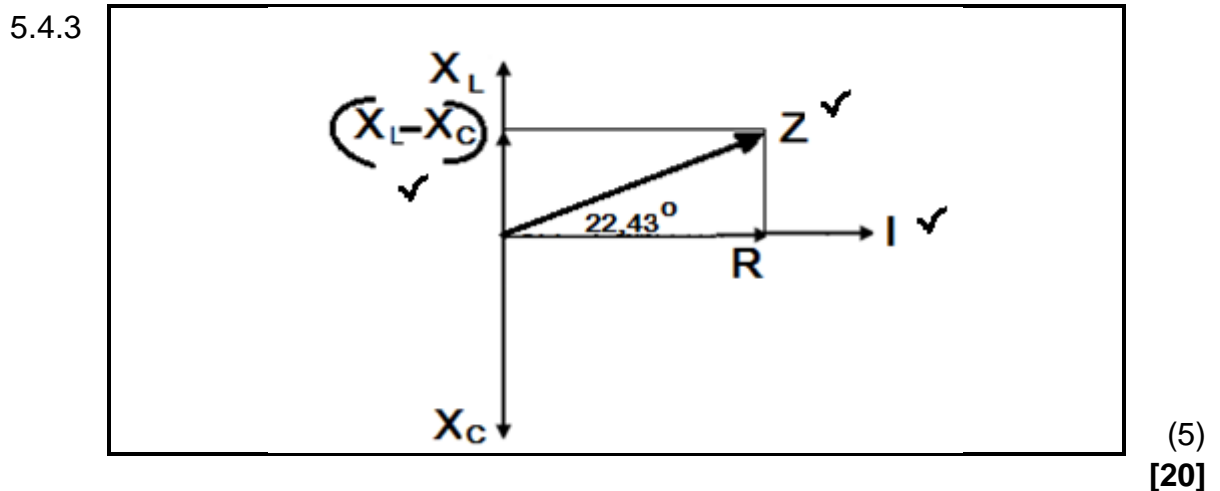

QUESTION 6: LOGIC

6.1 The Product of Sum notation is where the Boolean expression is made up of a number of sum terms, separated by a product sign. ✓
 $Q = (A + B) \cdot (A + C) \cdot (B + C)$ ✓

The Sum of Product notation is where the Boolean expression is made up of a number of product terms, separated by a sum sign. ✓
 $Q = A \cdot B + A \cdot C + B \cdot C$ ✓

(4)

6.2

A	B	C	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

✓✓

$$\bar{A}BC + A\bar{B}C + AB\bar{C} + ABC = Q$$

$$BC(\bar{A} + A) + \bar{A}BC + ABC = Q \quad \checkmark$$

$$BC + \bar{A}BC + ABC = Q$$

$$C(B + A\bar{B}) + ABC = Q \quad \checkmark$$


$$C(B + A) + ABC = Q$$

$$BC + AC + ABC = Q \quad \checkmark$$

$$BC + A(\bar{C} + BC) = Q$$


$$BC + A(C + B) = Q \quad \checkmark$$

$$BC + AC + AB = Q \quad \checkmark$$

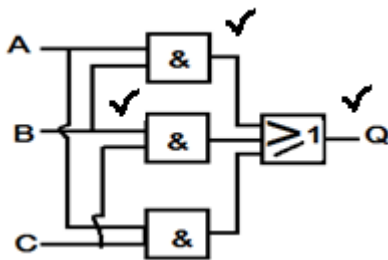

(10)

6.3 6.3.1

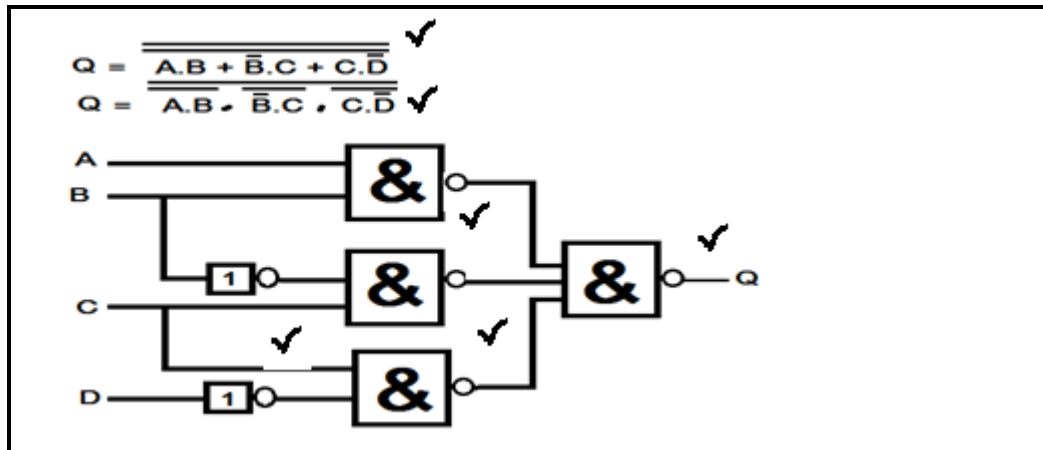

(6)
[20]

QUESTION 7: COMMUNICATIONS


- 7.1 7.1.1 1. Mixer ✓
2. Local oscillator ✓
3. AF amplifier ✓

(3)

7.1.2 FM receiver ✓

(1)

7.2

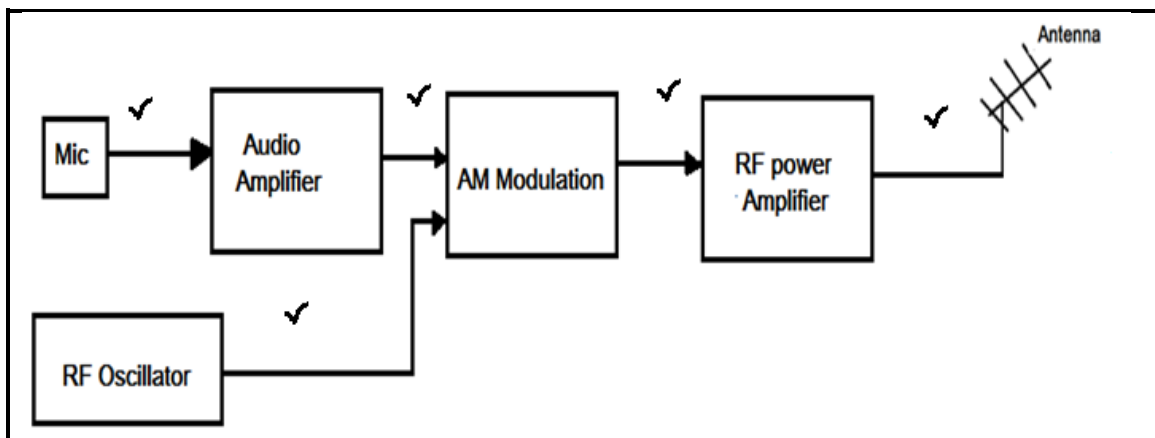

(5)

7.3 Foster-Seeley discriminators are sensitive to both frequency and amplitude variations, unlike some detectors. ✓ The discriminator compares the incoming FM signal against a reference signal ✓ and the difference between the two signals is the original audio signal. ✓

(3)

7.4 The main function is to connect transmitters and receivers to electromagnetic waves. ✓✓

(2)

- 7.5
- Its unsophisticated signal can be detected with simple equipment. ✓
 - It uses a narrower bandwidth than FM. ✓

(2)

- 7.6
- Amplitude modulation ✓
 - Frequency modulation ✓
 - Pulse modulation ✓

(3)
[20]

TOTAL: 200